

ECE 457- Microwave Devices and Circuits


Spring 2024

Homework #2 - Transmission lines


Due: Friday Feb 16th 5pm

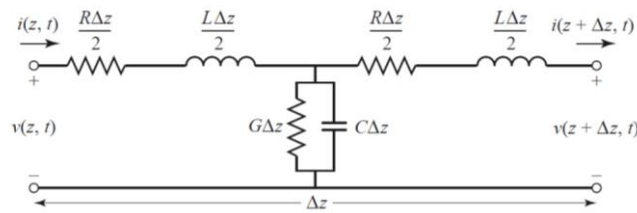1. Pozar, 2.7.


Show that the T -model of a transmission line shown in the accompanying figure also yields the telegrapher equations derived in Section 2.1.



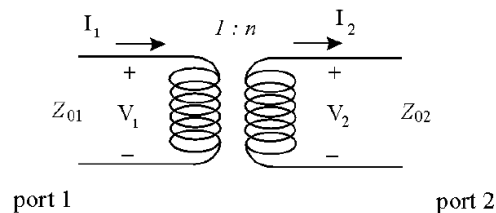2. A lossless transmission line of characteristic impedance $Z_0 = 100\Omega$ is terminated with a load impedance of $Z_L = 110 + j70\Omega$. The transmission line is 0.692λ long.
 - (a) Determine the reactance which, if connected across the input terminals to the line, makes the total impedance purely resistive.
 - (b) Under this condition, what is the input impedance of the line?
 - (c) Suggest a method for realizing this required reactance using only transmission lines.
3. Consider an ideal transformer with a turns ratio of $1 : n$ connecting two transmission lines, Z_{01} and Z_{02} , as shown below:






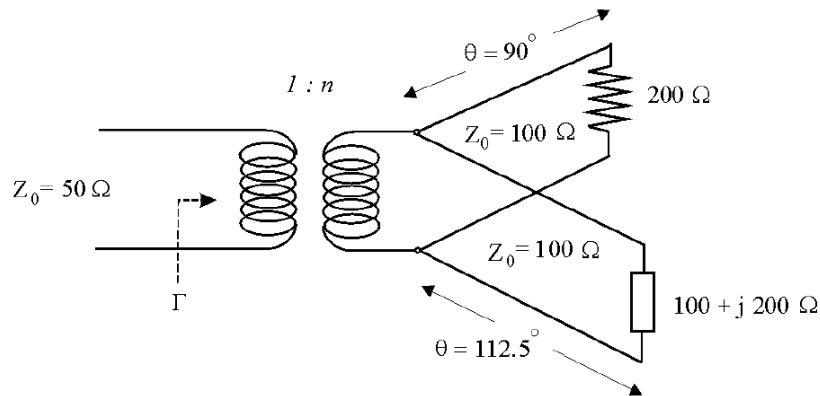- (a) Find the reflection and transmission coefficient of the transformer for a wave incident from the left (on transmission line Z_{01}). Express your answer in terms of the normalized impedance $z = Z_{02}/Z_{01}$ and the turns ratio, n .
- (b) Consider the circuit shown below. Find the turns ratio for the transformer that *minimizes* the magnitude of the reflection coefficient, Γ .



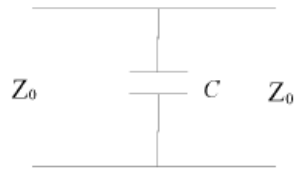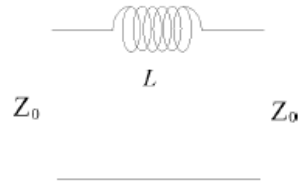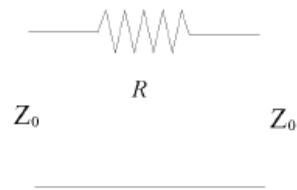
4. Consider the sections of transmission line with four different lumped elements shown below.

- Find the reflection coefficient at each lumped element for a wave incident from the left (assume the line is infinitely long in both directions).
- Find simplified expressions for Γ that apply when R , G , L , and C are small (but non-zero).
- If the incident waveform is a pulse, sketch what the reflected pulse would look like in each case.



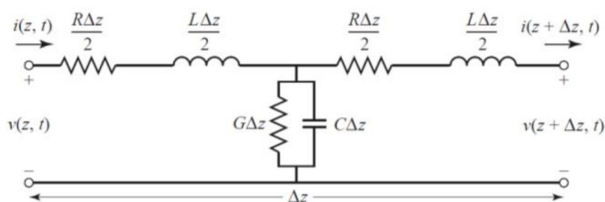1. Pozar, 2.7.

Show that the T -model of a transmission line shown in the accompanying figure also yields the telegrapher equations derived in Section 2.1.



$$\text{KVL: } v(z, t) - i(z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z, t)}{dt} - i(z + \Delta z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z + \Delta z, t)}{dt} - v(z + \Delta z, t) = 0$$


$$\text{voltage through inductor: } V_{\text{ind}} = L \frac{di}{dt}$$

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = \lim_{\Delta z \rightarrow 0} \frac{-i(z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z, t)}{dt} - i(z + \Delta z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z + \Delta z, t)}{dt}}{\Delta z}$$

$$= \frac{\partial v(z, t)}{\partial z} = -i(z, t) \frac{R}{2} - \frac{L}{2} \frac{di(z, t)}{dt} - i(z, t) \frac{R}{2} - \frac{L}{2} \frac{di(z, t)}{dt}$$

$$\boxed{\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{di(z, t)}{dt}}$$

KCL:

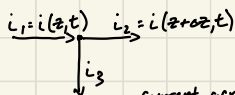

$$\text{current across capacitor: } i = C \frac{dv}{dt}$$

$$i(z, t) = i_3 + i_2(z + \Delta z, t) \quad \text{where } i_3 = V_3 / Z_3 = \left(v(z, t) - i(z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z, t)}{dt} \right) (\Delta z G) + C \Delta z \frac{\partial}{\partial t} \left(v(z, t) - i(z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z, t)}{dt} \right)$$

$$i_2(z + \Delta z, t) - i(z, t) = -i_3$$

$$\lim_{\Delta z \rightarrow 0} \frac{i_2(z + \Delta z, t) - i(z, t)}{\Delta z} = \lim_{\Delta z \rightarrow 0} \frac{-i_3}{\Delta z}$$


$$\lim_{\Delta z \rightarrow 0} \frac{-i_3}{\Delta z} = - \left[\left(v(z, t) - i(z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z, t)}{dt} \right) G + C \frac{\partial}{\partial t} \left(v(z, t) - i(z, t) \frac{R\Delta z}{2} - \frac{L\Delta z}{2} \frac{di(z, t)}{dt} \right) \right]$$

$$\frac{\partial i(z, t)}{\partial z} = \lim_{\Delta z \rightarrow 0} \frac{-i_3}{\Delta z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

$$\rightarrow \boxed{\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}}$$

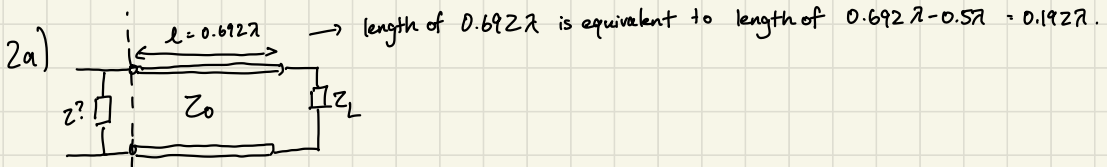2. A lossless transmission line of characteristic impedance $Z_0 = 100 \Omega$ is terminated with a load impedance of $Z_L = 110 + j70 \Omega$. The transmission line is 0.692λ long.

- Determine the reactance which, if connected across the input terminals to the line, makes the total impedance purely resistive. $Z_L = 1.1 + 0.7j$
- Under this condition, what is the input impedance of the line?
- Suggest a method for realizing this required reactance using only transmission lines.




$$\Gamma_o = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{110 + j70 - 100}{110 + j70 + 100} = \frac{10 + j70}{210 + j70} = \frac{1 + j7}{21 + j7} \Rightarrow 0.33e^{j1.234}$$

$$Z_{in}(d) = Z_0 \frac{1 + \Gamma_o e^{-j2\beta d}}{1 - \Gamma_o e^{-j2\beta d}} \quad \text{where } \beta d = \frac{2\pi}{\lambda} \cdot 0.192\lambda = 0.384\pi$$

$$Z_{in}(d) \approx 96.08 - 65.969j \quad Y_{in} = 0.7 + 0.48j$$

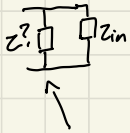\Rightarrow the line can be simplified to this



what is $Z?$ such that $Z? \parallel Z_{in}$ is purely resistive

parallel impedances can be viewed as inverse of the sum of admittances

$$\frac{1}{Z_T} = \frac{1}{Z?} + \frac{1}{Z_{in}}$$

$$\frac{1}{Z_T} = \frac{1}{jX} + \frac{1}{Z_{in}}$$

$$\therefore Z_T = R = \frac{Z_{in} jX}{jX + Z_{in}} \quad \text{complex}$$

$$Z_{in} jX = X(96.08j + 65.969j)$$

$$jX + Z_{in} = 96.08 - 65.969j + jX$$

$$96.08 + (X - 65.969)j$$

$$\therefore Z_T = \frac{(96.08Xj + 65.969X)(96.08 - (X - 65.969)j)}{(96.08)^2 + (X - 65.969)^2}$$

$$= 96.08^2 Xj + 96.08X(X - 65.969) + 65.969X(96.08) - 65.969X(X - 65.969)j$$

in order for Z_T to be real, then imaginary components have to sum to 0.

$$96.08^2 Xj - 65.969 X^2 j + 65.969^2 Xj = 0$$

$$X(96.08^2 - 65.969X + 65.969^2) = 0$$

$$X = 0 \quad 96.08^2 + 65.969^2 = 65.969 X$$

trivial case, since $Z_T = 0$

$$X = \frac{96.08^2 + 65.969^2}{65.969}$$

$$X \approx 205.906 \Omega$$

Reactance of around $205.906 j \Omega$ needed

b) Using a parallel calculation:

$$Z_{in, total} = \frac{Z_{in, line} \cdot jX}{jX + Z_{in, line}} \approx \boxed{141.375 \Omega}$$

c) This reactance can be realized with an open stub transmission line in parallel.

$$\begin{aligned} Z_{in, open} &= -jZ_0 \cot \beta d \\ &= -j(100) \cot\left(\frac{2\pi}{\lambda}(l')\right) \end{aligned}$$

$$Z_{in, open} = -j100 \cot(2\pi l') = 205.906 j$$

$$\cot(2\pi l') = \frac{-205.906}{100}$$


$$2\pi l' = \arctan\left(\frac{-100}{205.906}\right)$$

$$l' = \frac{1}{2\pi} \left(\arctan\left(\frac{-100}{205.906}\right) + \pi \right)$$

$$l' \approx 0.428 \lambda$$

\therefore an open stub t-line with a length of 0.428λ can be used to realize the reactance found in part a.

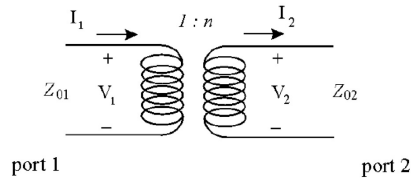3. Consider an ideal transformer with a turns ratio of $1 : n$ connecting two transmission lines, Z_{01} and Z_{02} , as shown below:



- (a) Find the reflection and transmission coefficient of the transformer for a wave incident from the left (on transmission line Z_{01}). Express your answer in terms of the normalized impedance $z = Z_{02}/Z_{01}$ and the turns ratio, n .

a) Ideal transformer:

$$\frac{V_1}{n_1} = \frac{V_2}{n_2} \quad \text{where} \quad \frac{n_1}{n_2} = \frac{1}{n} \quad \therefore n_2 = n \cdot n_1$$

$$\therefore V_2 = V_1 \frac{n_2}{n_1} \rightarrow V_2 = V_1 \frac{n \cdot n_1}{n_1} \rightarrow V_2 = n \cdot V_1$$


$$P_{\text{left}} = P_{\text{right}}$$

$$V_1 i_1 = V_2 i_2$$

$$V_1 i_1 = n V_1 i_2$$

$$i_1 = n i_2$$

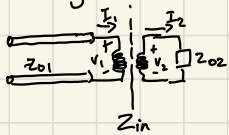Assuming that line 2 is infinite, we can draw the line as



$$Z_{\text{in}} = \frac{V_1}{I_1} \quad i_1 = n i_2$$

$$= \frac{V_2}{n} \cdot \frac{1}{n i_2}$$

$$= \frac{V_2}{i_2} \cdot \frac{1}{n^2}$$

$$Z_{\text{in}} = Z_{02} \cdot \frac{1}{n^2}$$

$$Z_{\text{in}} = \frac{Z_{02}}{n^2}$$


$$\Gamma = \frac{Z_{\text{in}} - Z_{01}}{Z_{\text{in}} + Z_{01}} \quad \text{where} \quad Z_{\text{in}} = \frac{Z_{02}}{n^2}$$

$$= \frac{\frac{Z_{02}}{n^2} - Z_{01}}{\frac{Z_{02}}{n^2} + Z_{01}} \cdot \frac{\frac{1}{Z_{01}}}{\frac{1}{Z_{01}}}$$

$$= \frac{\frac{z}{n^2} - 1}{\frac{z}{n^2} + 1}$$


$$\Gamma = \frac{z - n^2}{z + n^2}$$
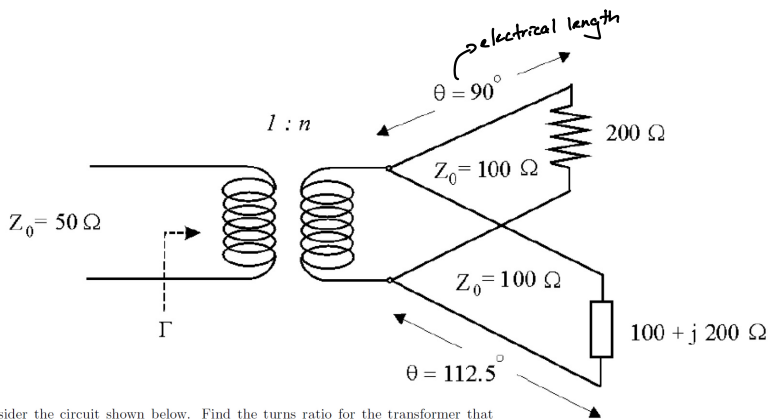
$$T = 1 + \Gamma \therefore T = \frac{2z}{z + n^2}$$



(b) Consider the circuit shown below. Find the turns ratio for the transformer that minimizes the magnitude of the reflection coefficient, Γ .

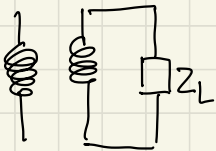b) first we must determine the load impedance



the line terminated w/ 200Ω

$$\text{has a } Z_{in,1} = Z_0 \frac{1 + \Gamma_1 e^{j2\beta d}}{1 - \Gamma_1 e^{-j2\beta d}} \text{ where } \Gamma_1 = \frac{Z_{L,1} - 100}{Z_{L,1} + 100} = \frac{100}{300} = \frac{1}{3}$$

$$Z_{in,1} = 100 \left(\frac{1 + \frac{1}{3} e^{-j2(90^\circ)}}{1 - \frac{1}{3} e^{-j2(90^\circ)}} \right)$$

$$Z_{in,1} = 100 \left(\frac{1 + \frac{1}{3} e^{-j(180^\circ)}}{1 - \frac{1}{3} e^{-j(180^\circ)}} \right)$$

$$= 100 \left(\frac{\frac{2}{3}}{\frac{4}{3}} \right) = 100 \left(\frac{1}{2} \right) = 50 \Omega$$

$$Z_{in,2} = Z_0 \frac{1 + \Gamma_2 e^{-j2\beta d}}{1 - \Gamma_2 e^{-j2\beta d}} \text{ where } \Gamma_2 = \frac{100 + 200j - 100}{100 + 200j + 100}$$

$$\text{where } 2 \cdot \beta d = 2 \cdot 112.5^\circ = 225^\circ = \frac{200j}{200 + 200j}$$

$$Z_{in,2} = Z_0 \frac{1 + \Gamma_2 e^{-j225^\circ}}{1 - \Gamma_2 e^{-j225^\circ}}$$

$$\Gamma_2 = \frac{j(1-j)}{2}$$

$$Z_{in,2} = 100 \frac{1 + \sqrt{2} e^{j45^\circ} e^{-j225^\circ}}{1 - \sqrt{2} e^{j45^\circ} e^{-j225^\circ}}$$

$$\Gamma_2 = \frac{j+1}{2}$$


$$= 100 \frac{1 + \frac{\sqrt{2}}{2} e^{-j180^\circ}}{1 - \frac{\sqrt{2}}{2} e^{-j180^\circ}}$$

$$= 100 \frac{1 - \frac{\sqrt{2}}{2}}{1 + \frac{\sqrt{2}}{2}}$$

$$= 100 \left(\frac{2 - \sqrt{2}}{2 + \sqrt{2}} \right)$$


$$\approx 17.157 \Omega$$

now the lines can be drawn as:

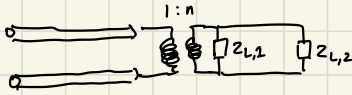

$$\therefore Z_{L \text{ total}} = \frac{Z_{L,1} \cdot Z_{L,2}}{Z_{L,1} + Z_{L,2}} = \frac{50 \cdot 17.157}{50 + 17.157} \approx 12.774 \Omega$$

now the line is drawn as:

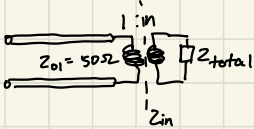


we know from part a) $Z_{in} = \frac{Z_{02}}{n^2}$ where $Z_{02} = Z_{total}$

$$\therefore Z_{in} = \frac{Z_{total}}{n^2}$$

$$\therefore Z_{in} = \frac{12.774}{n^2}$$

$$\Gamma = \frac{Z_{in} - Z_{01}}{Z_{in} + Z_{01}} = \frac{\frac{12.774}{n^2} - 50}{\frac{12.774}{n^2} + 50}$$
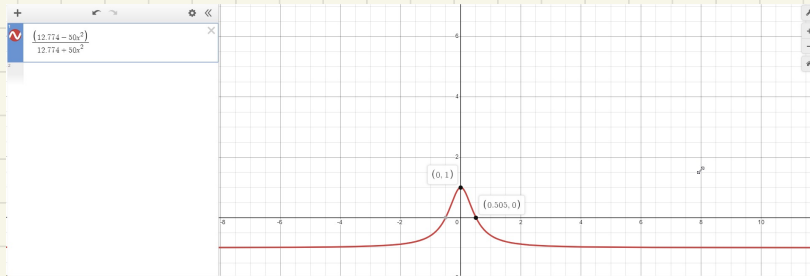
$$\Gamma = \frac{12.774 - 50n^2}{12.774 + 50n^2} \text{ find } n \text{ that minimizes this}$$










we can see that Γ is minimized (to 0) when $n \approx \frac{1}{2}$

\therefore coil 1 should have twice as many turns as coil 2.

i.e. a 2:1 ratio

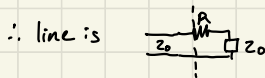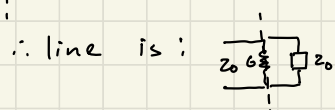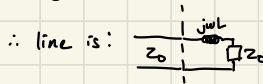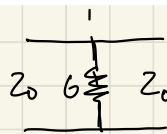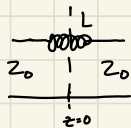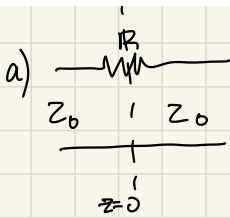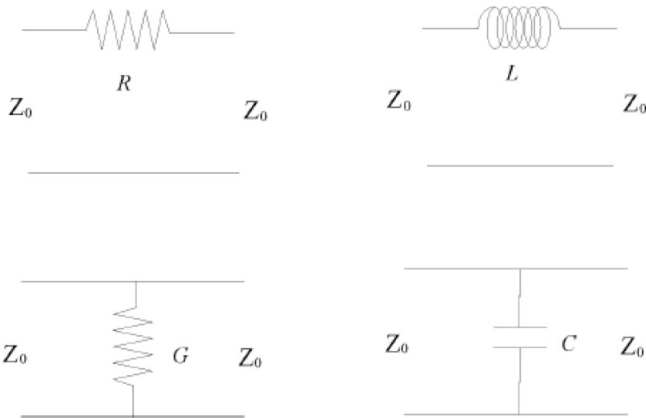4. Consider the sections of transmission line with four different lumped elements shown below.

- Find the reflection coefficient at each lumped element for a wave incident from the left (assume the line is infinitely long in both directions).
- Find simplified expressions for Γ that apply when R, G, L , and C are small (but non-zero).
- If the incident waveform is a pulse, sketch what the reflected pulse would look like in each case.



where $Z_{total} = R + Z_0$

$$\therefore \Gamma = \frac{R + Z_0 - Z_0}{R + Z_0 + Z_0} = \frac{R}{R + 2Z_0}$$

$$\boxed{\Gamma = \frac{R}{R + 2Z_0}}$$

where $Z_{total} = j\omega L + Z_0$

$$\therefore \Gamma = \frac{j\omega L + Z_0 - Z_0}{j\omega L + Z_0 + Z_0}$$

$$\boxed{\Gamma = \frac{j\omega L}{j\omega L + 2Z_0}}$$



$$\therefore Z_{tot} = \frac{Z_0}{\frac{1}{G} + Z_0} = \frac{Z_0}{1 + GZ_0}$$

$$\Gamma = \frac{\frac{Z_0}{1 + GZ_0} - Z_0}{\frac{Z_0}{1 + GZ_0} + Z_0} \cdot \frac{1 + GZ_0}{1 + GZ_0}$$

$$\Gamma = \frac{Z_0 - Z_0 - GZ_0^2}{Z_0 + Z_0 + GZ_0^2}$$

$$\Gamma = \frac{1 - 1 - GZ_0}{1 + 1 + GZ_0}$$
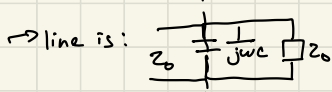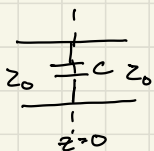
$$\boxed{\Gamma = \frac{-GZ_0}{2 + GZ_0}}$$



$$\therefore Z_{total} = \frac{Z_0}{\frac{1}{j\omega C} + Z_0} = \frac{Z_0}{1 + j\omega C Z_0}$$

$$\Gamma = \frac{\frac{Z_0}{1 + j\omega C Z_0} - Z_0}{\frac{Z_0}{1 + j\omega C Z_0} + Z_0} = \frac{1 - 1 - j\omega C Z_0}{1 + 1 + j\omega C Z_0} = \boxed{\Gamma = \frac{-j\omega C Z_0}{2 + j\omega C Z_0}}$$

b) for $\Gamma = \frac{R}{R + 2Z_0}$ as $R \rightarrow 0$, Γ will also approach 0 since it will be a very small # divided by $2Z_0$.

$$\therefore \boxed{\Gamma_R \approx 0^+}$$

for $\Gamma_L = \frac{j\omega L}{j\omega L + 2Z_0}$ as $L \rightarrow 0$, Γ will also approach 0 since it will be a small number divided by $2Z_0$.

$$\therefore \boxed{\Gamma_L \approx 0^+}$$

it will also advance in phase by 90°


for $\Gamma_G = \frac{-GZ_0}{2 + GZ_0}$ as $G \rightarrow 0$, Γ will approach 0 since a very small # divided by 2 will also be small, however it will be a negative number since it will approach 0 from negative side.

$$\boxed{\Gamma_G \approx 0^-}$$

for $\Gamma_C = \frac{-j\omega C Z_0}{2 + j\omega C Z_0}$ as $C \rightarrow 0$, Γ will approach 0 since a very small # divided by 2 will also be small, just like Γ_G , it will be negative. return wave also lagged in phase 90° .


$$\boxed{\Gamma_C \approx 0^-}$$

c) The pulse for Γ_R will look like:

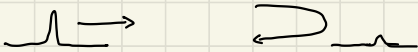


1) amplitude smaller

The pulse for Γ_L will look like

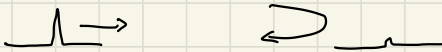

1) amplitude smaller


The pulse for Γ_G will look like

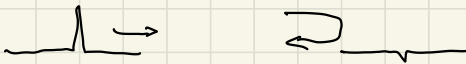

1) amplitude smaller

2) sign flip

The pulse for Γ_C will look like

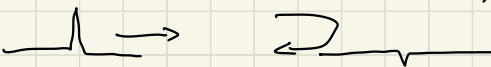

1) amplitude smaller

2) Sign flip.